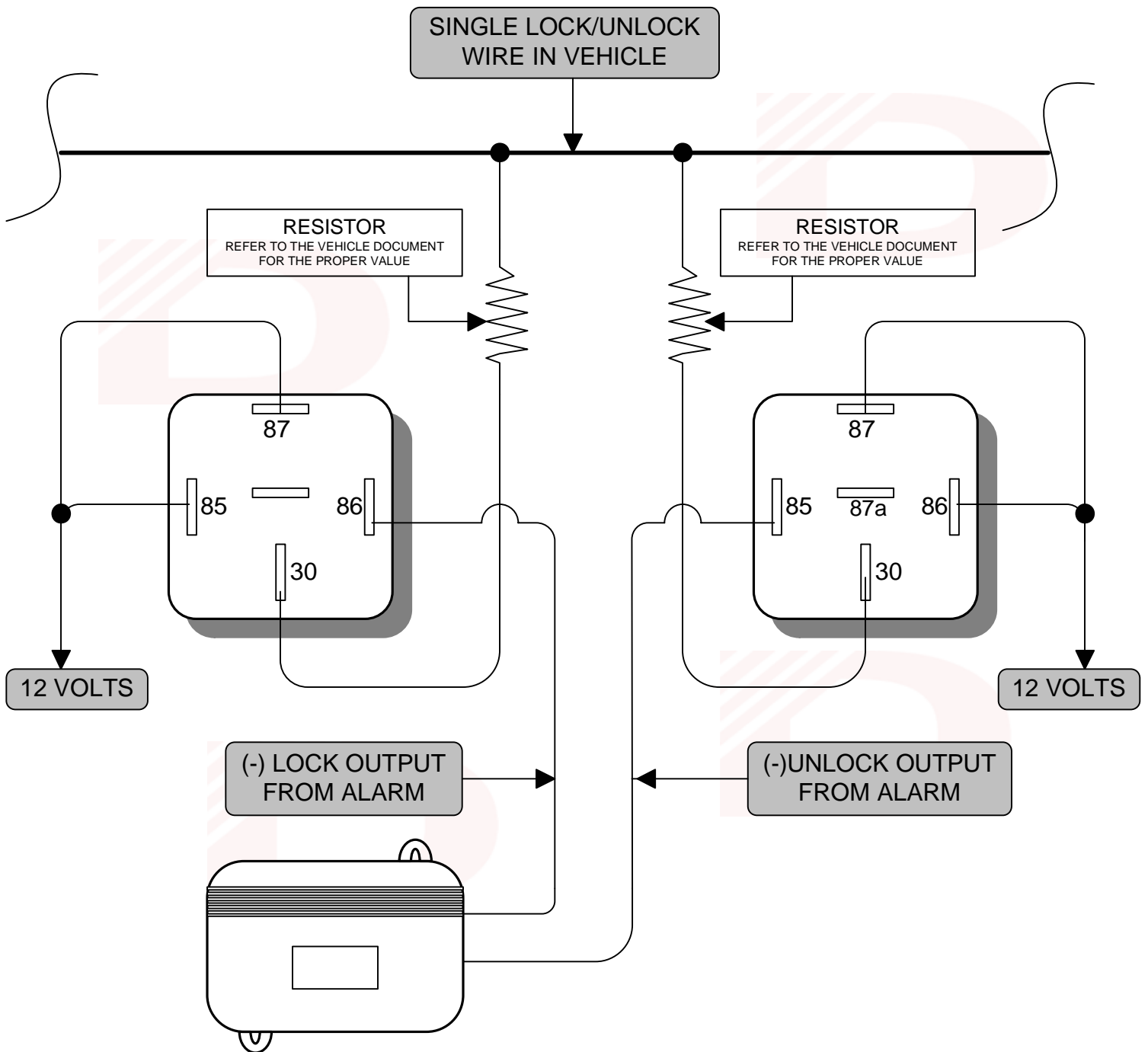




POSITIVE TRIGGER SINGLE WIRE MULTIPLEXED LOCK SYSTEM INTERFACE

Some vehicle use one wire to lock *and* unlock the doors. To interface properly with a keyless entry/alarm please follow the diagram below. Different vehicles will have different resistance values for lock and unlock, refer to the specific vehicle document for these values.



Note: Audiovox makes no representation or warranty with respect to the above information including its accuracy, completeness, or its freedom from third parties' proprietary rights. Audiovox disclaims all liability or responsibility for errors omissions therein or any decision made by the recipient in reliance thereon. The installer must verify any circuitry with the proper test equipment prior to installation.